

Lab 8

First of all, we're given an **RGB** LED, which is known for its '3 pins' instead of '1'. We can make a truth table solely off of how RGB works (using integers instead of 0-255).


R	G	B	Colour Output
0	0	0	Black
0	0	1	Blue
0	1	0	Green
0	1	1	Teal
1	0	0	Red
1	0	1	Purple
1	1	0	Yellow
1	1	1	White

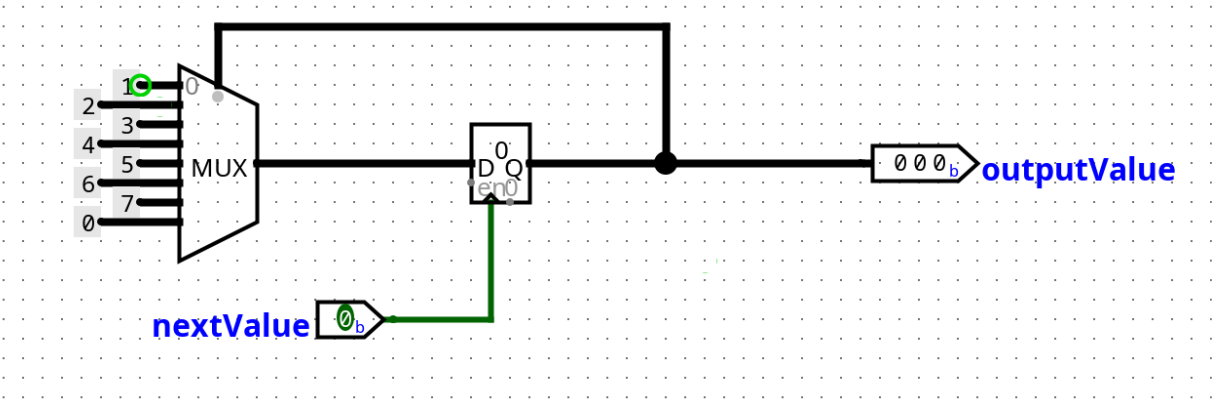With that, I can make a counter (0-7) and output its values to the three different pins of the LED, which works! Video will be attached on GitHub (I lied I forgot to record it)



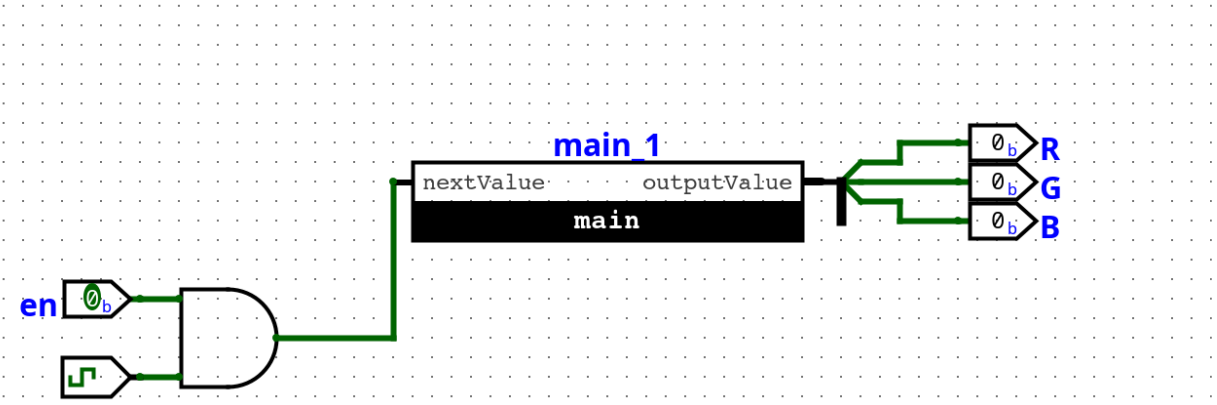

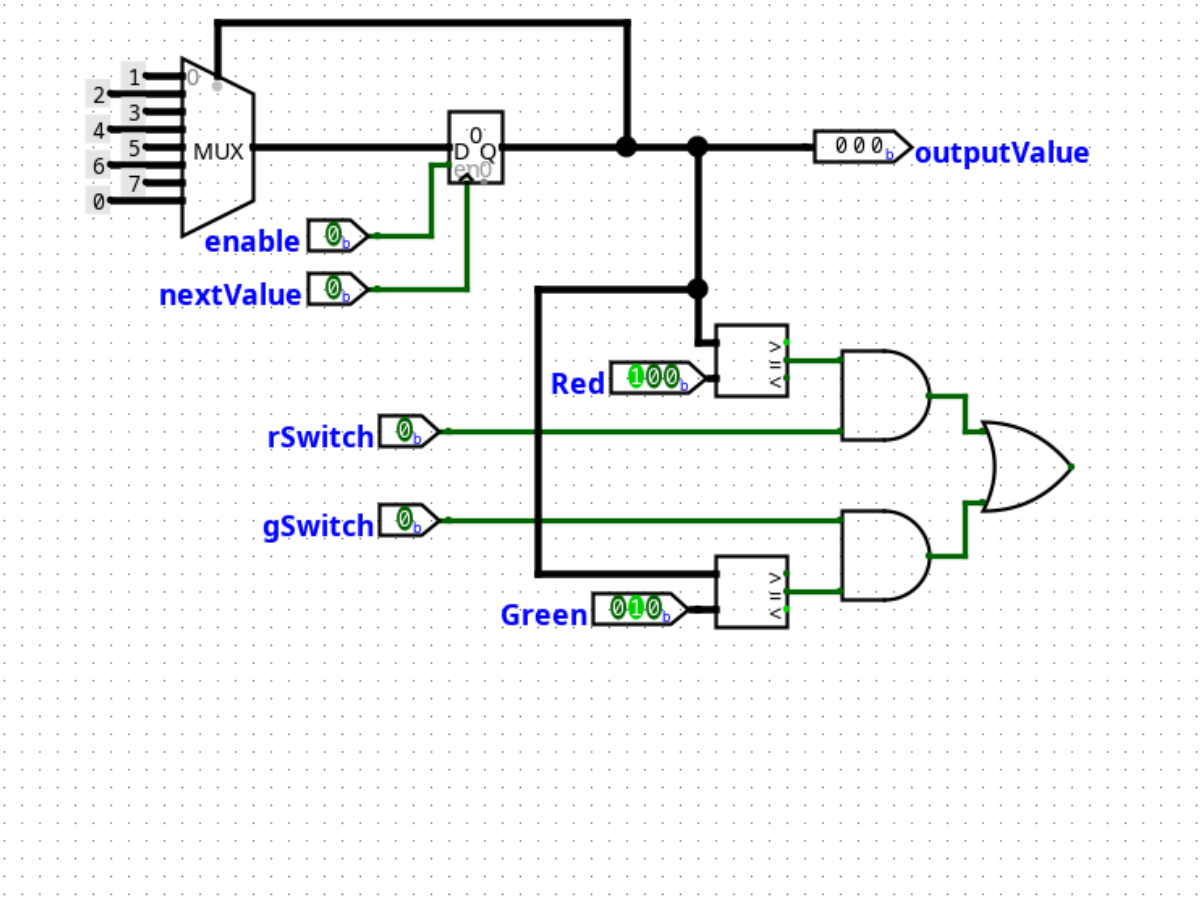..However, I ventured off of the beaten path, because I'm evil and the yellow brick road is BORING.



My goal was to trigger a stall whenever a switch was enabled--a stall at red would mean the redSwitch is enabled, and same vice versa. Buuut that would mean I'd need to add a counter to reference *my counter*, and that's where I got lost.