

LAB 7 PDF

And the random stuff I did


Yay!

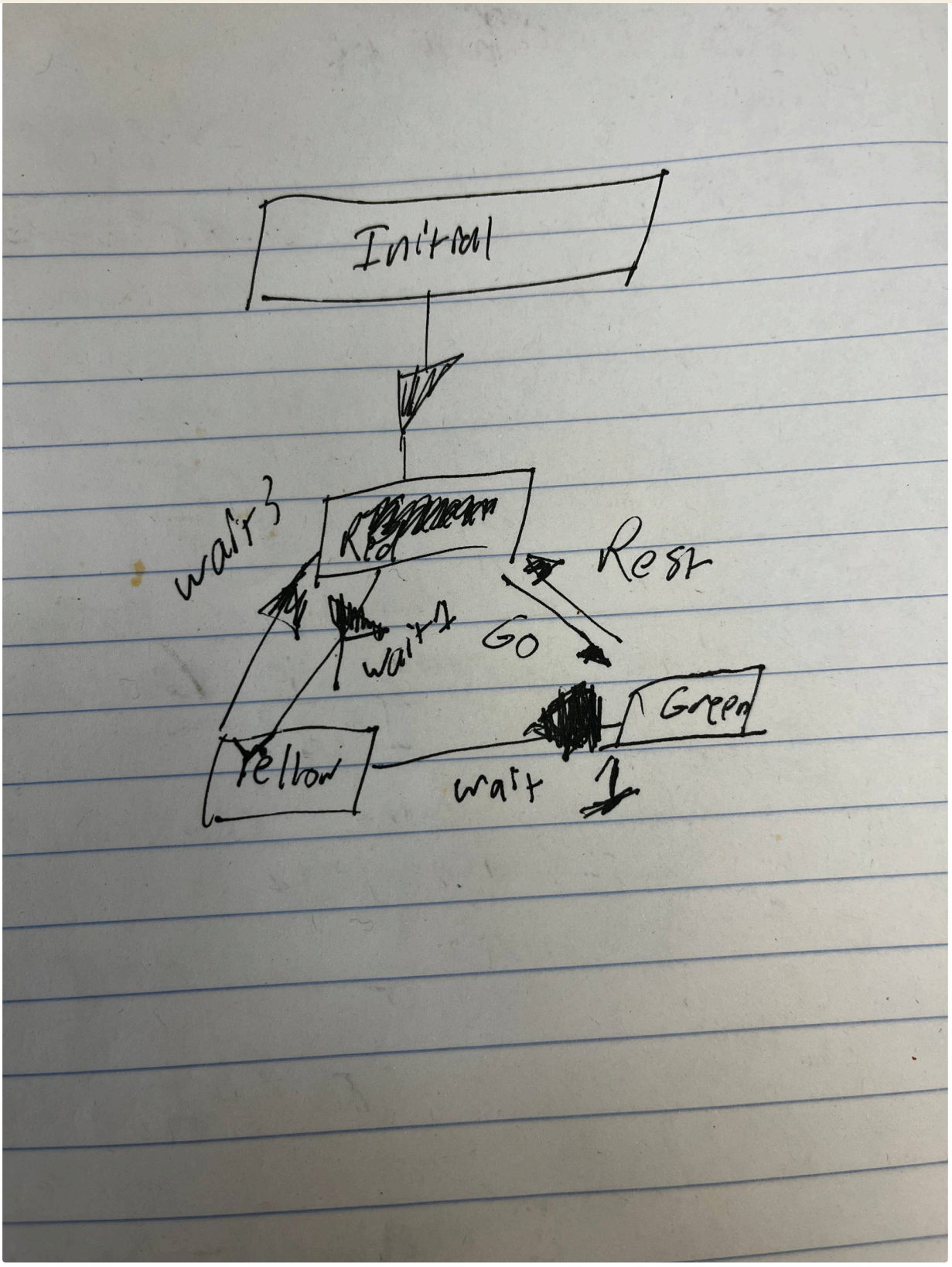

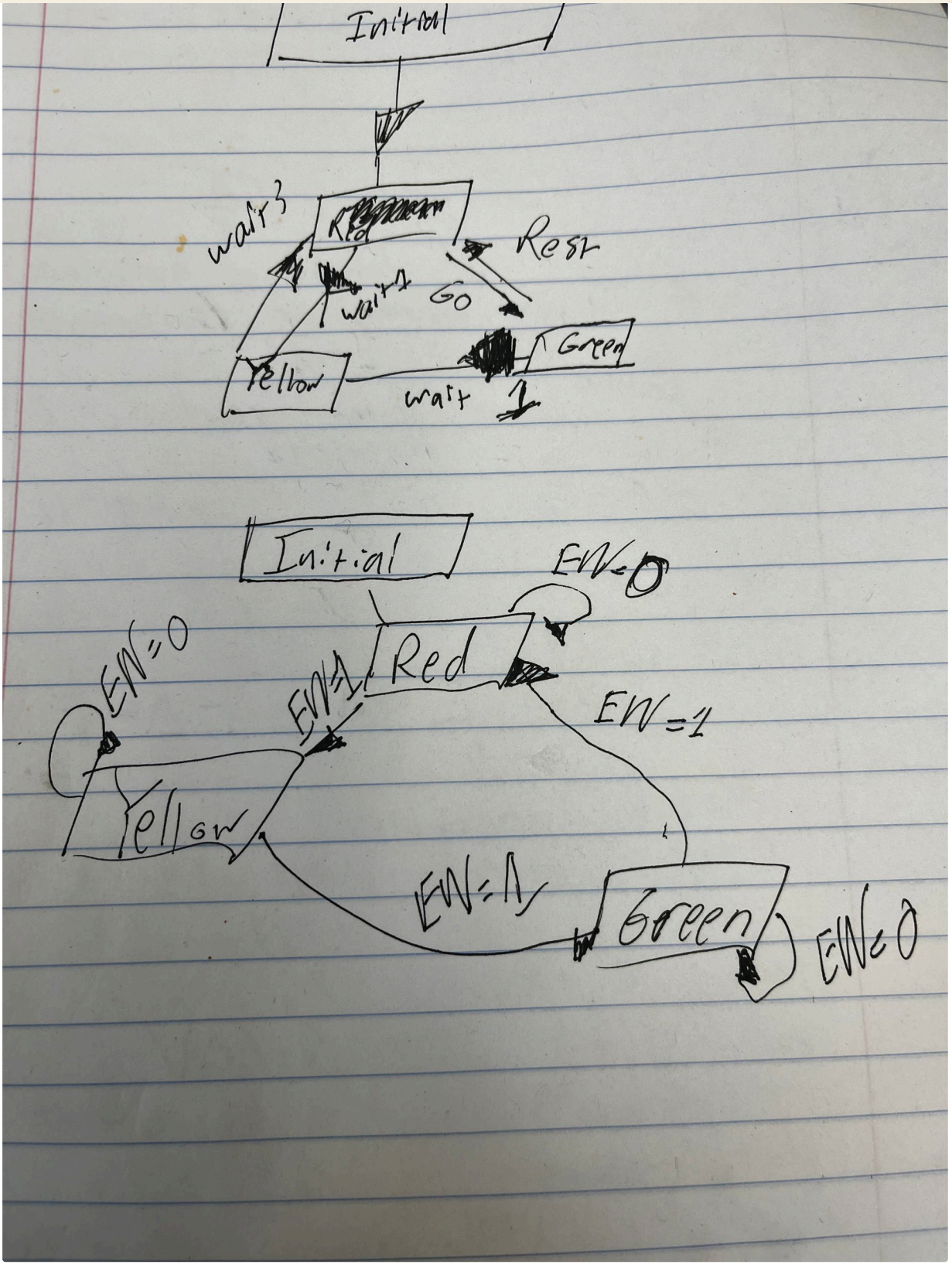**Initial Design, where I drew a triangle and added a wait to the transition instead of adding loops.



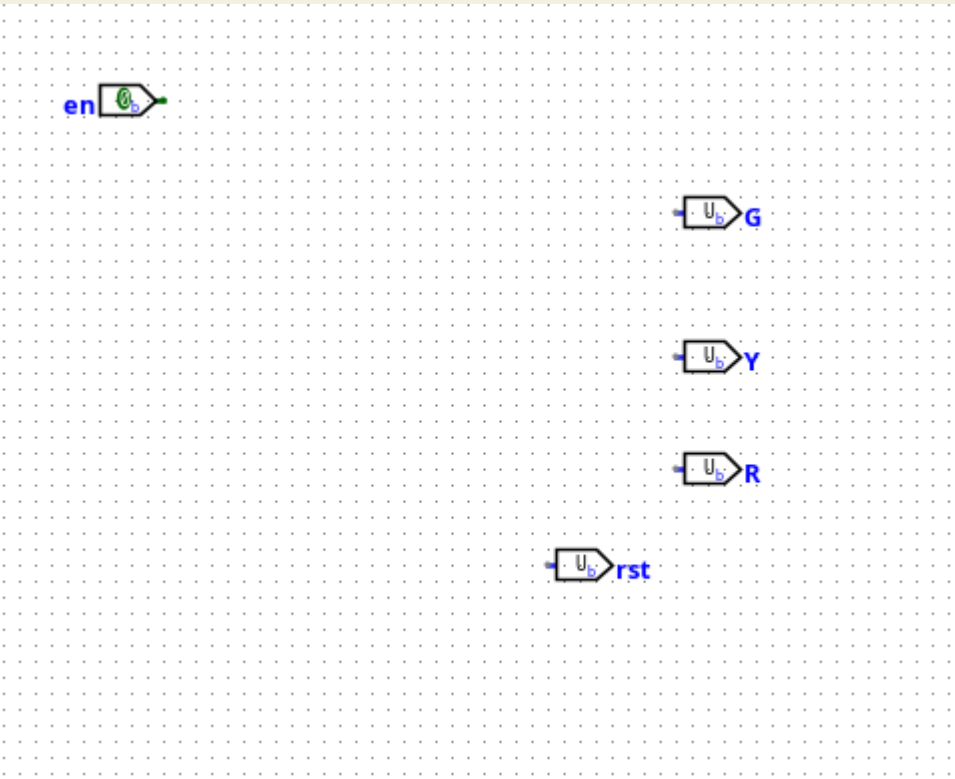
**Corrected my work with a reference from Dr. Martin using loops and a reset counter (with notations/Enables, along with a reset counter.)




Template we were given

Truth Table!! (Different states) ENABLE

State	0	1
0 0	0 0	0 1
0 1	0 1	1 0
1 0	1 0	0 0
1 1	--	--

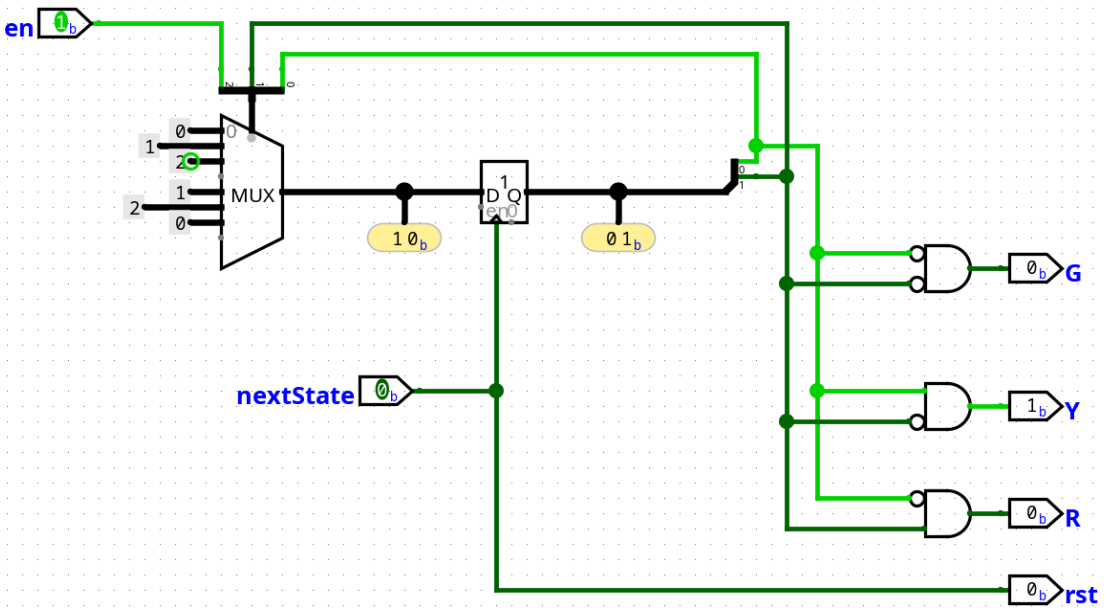
en
MUX
nextState
G
Y
R
rst

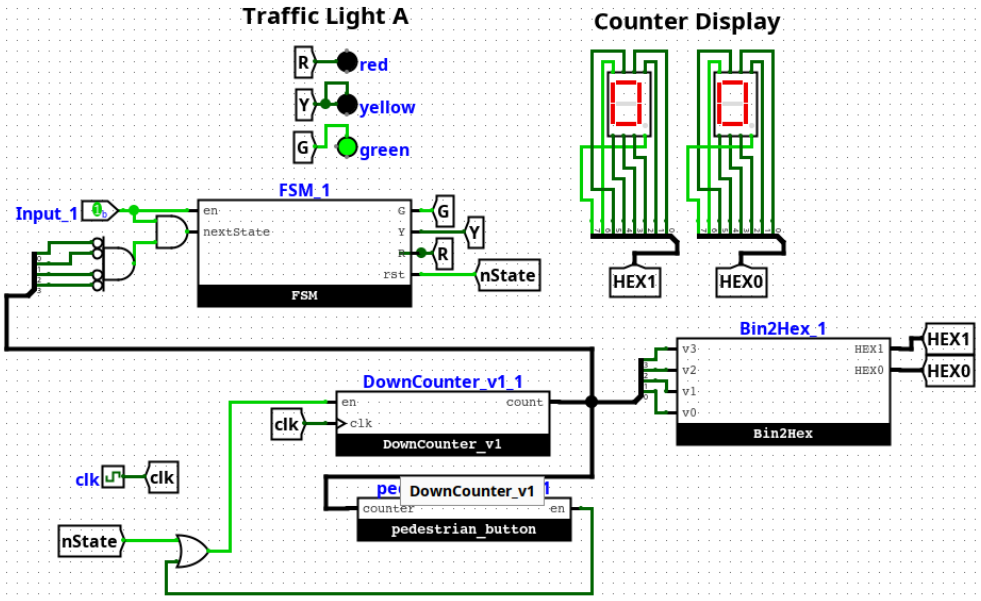
Traffic Light A
red
yellow
green
Counter Display
FSM_1
Input_1
nextState
FSM
nState
HEX1
HEX0
Bin2Hex_1
Bin2Hex
DownCounter_v1_1
DownCounter_v1
clk
pedestrian_button